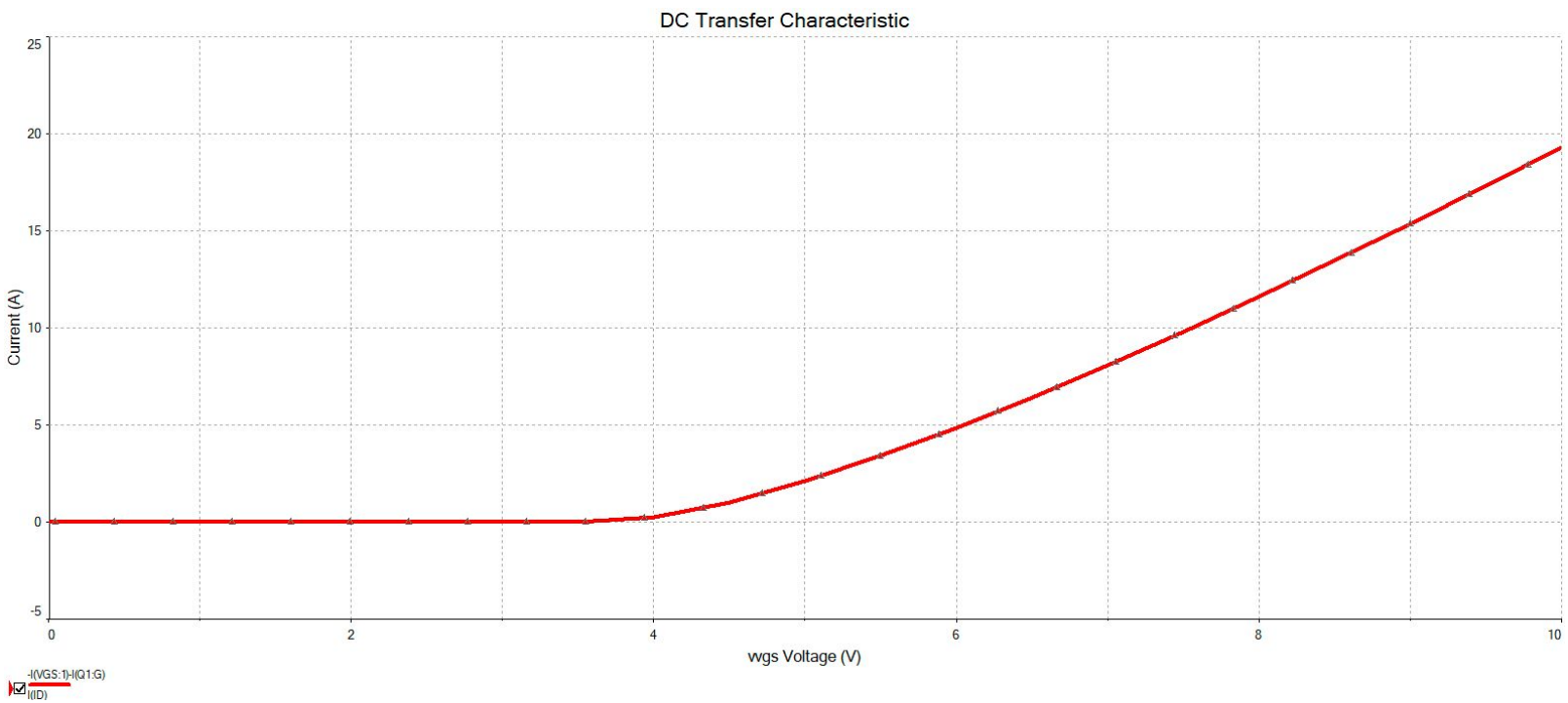
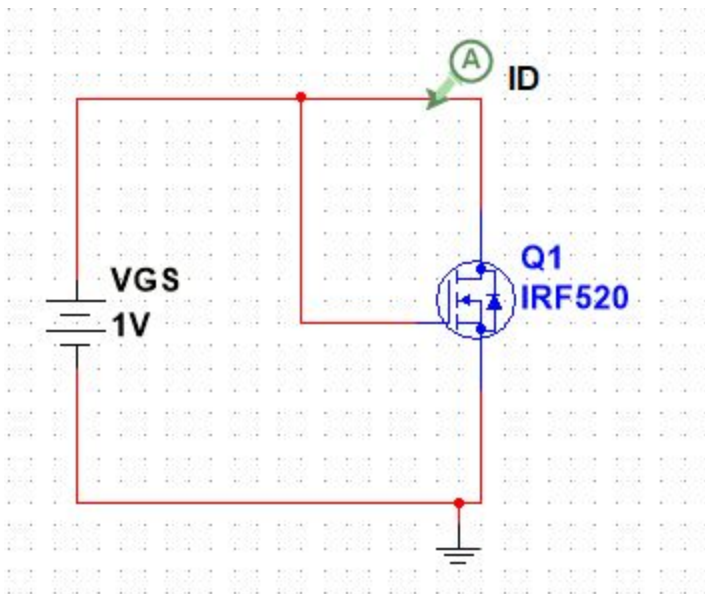
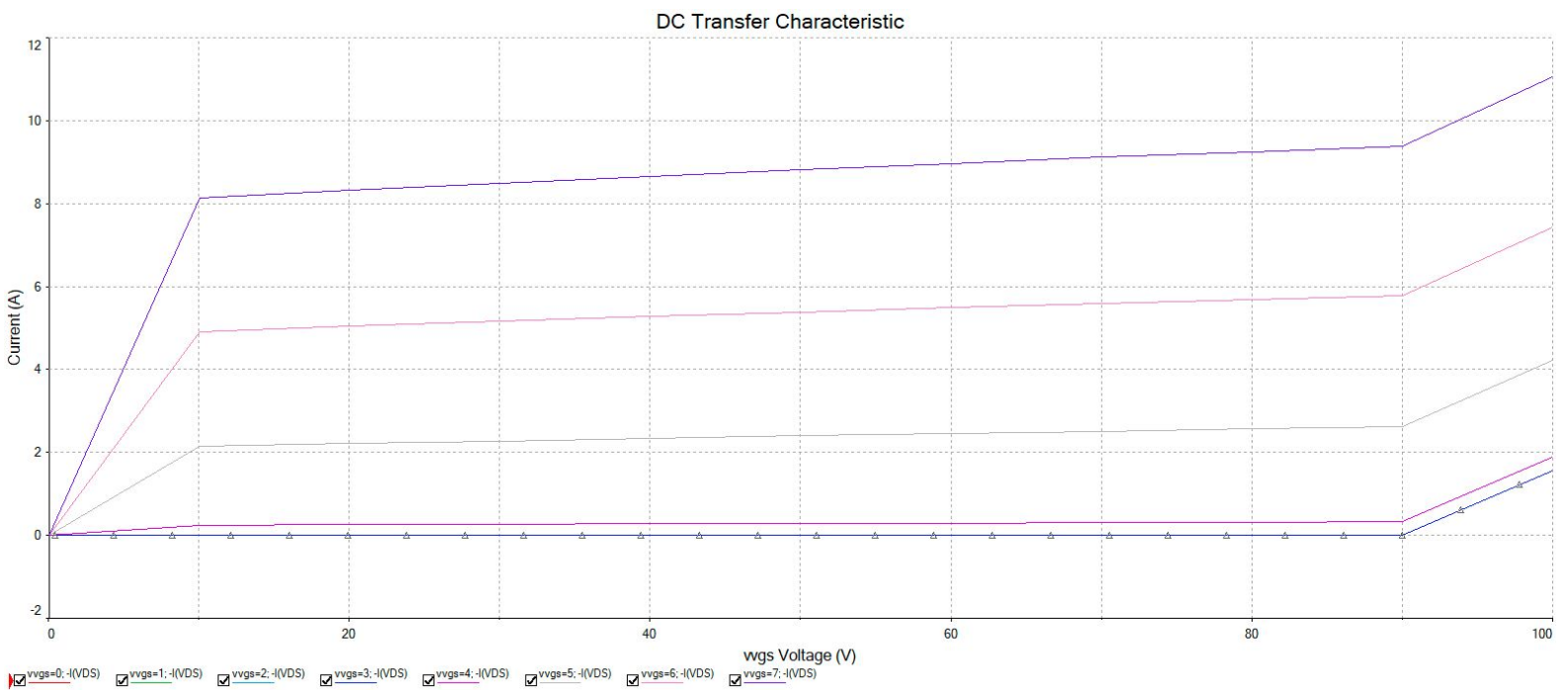
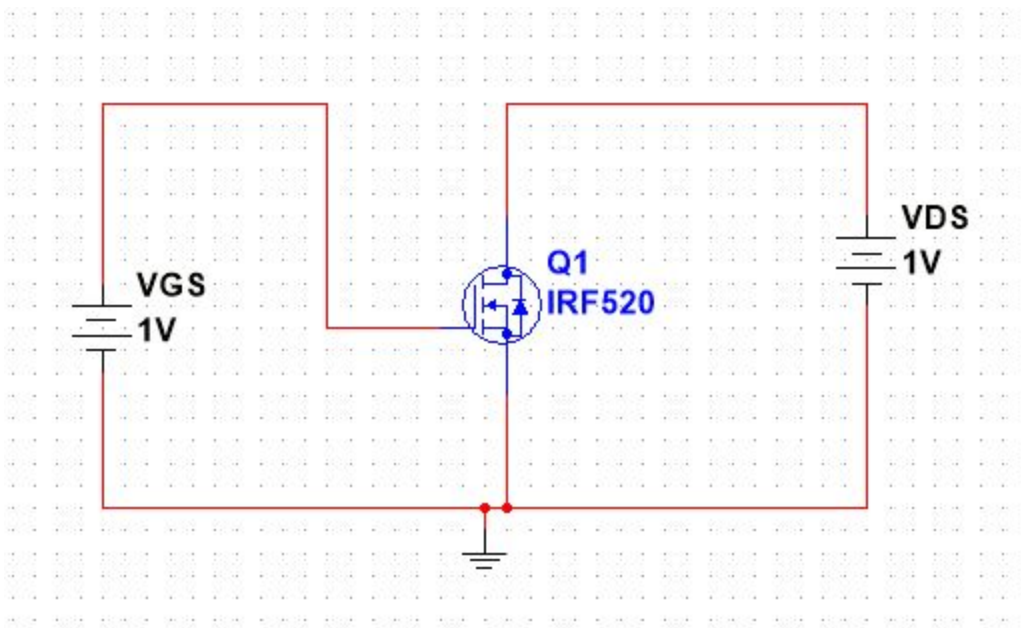
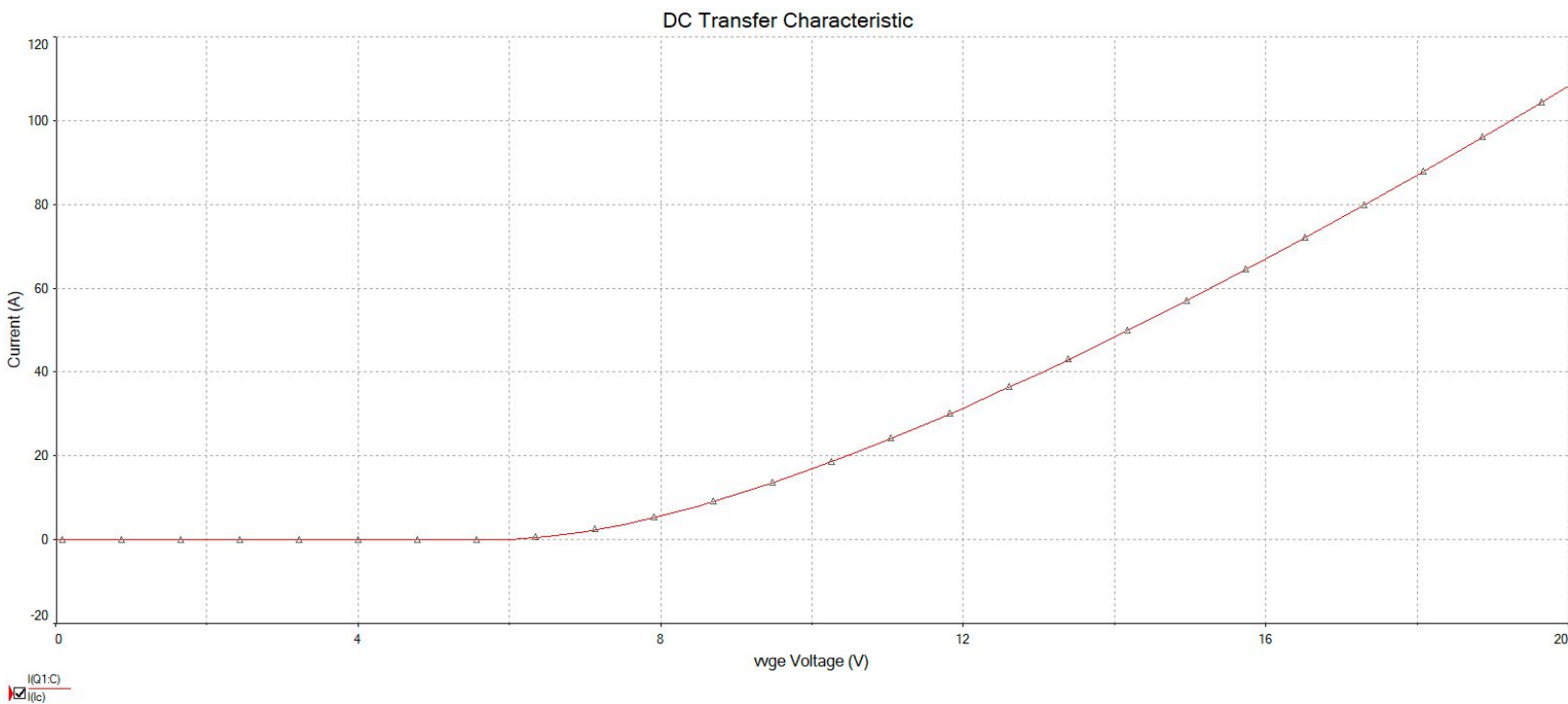
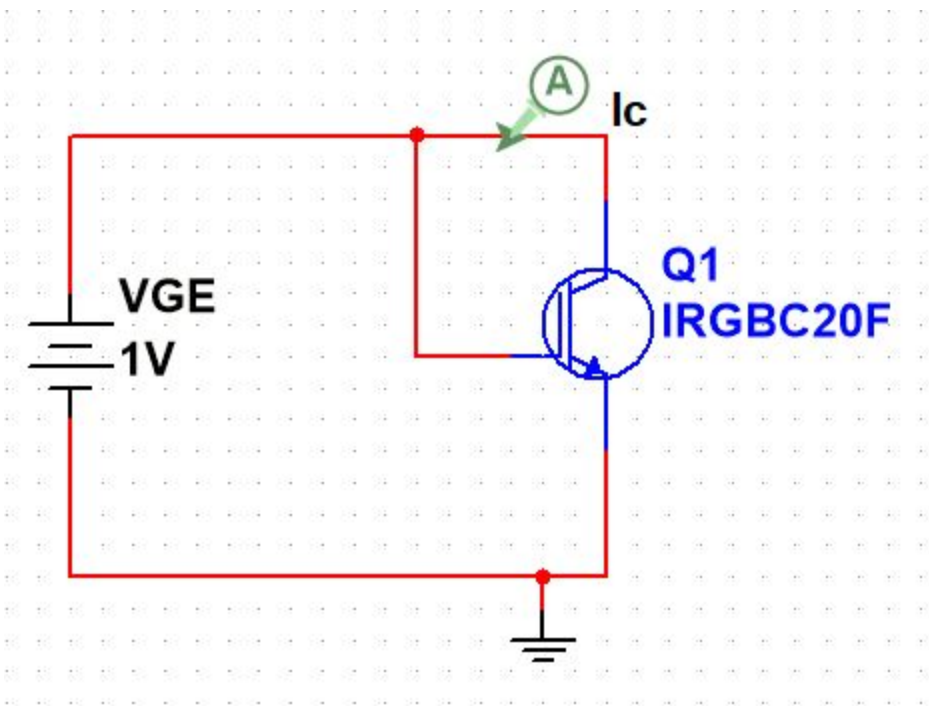


Experiment No. 2 A**Aim:** - To Simulate input and output of characteristics of Power MOSFETTransfer characteristics

Output characteristics

Experiment No. 2 B

Aim: - To Simulate input and output of characteristics of IGBT

Transfer characteristics

Output characteristics