

PED

## EXPERIMENT ~ 3


Name : RAHUL VEMURI

ROLL NO : 33



CLASS : D16A





# SINGLE-PHASE HALF-WAVE DIODE RECTIFIER

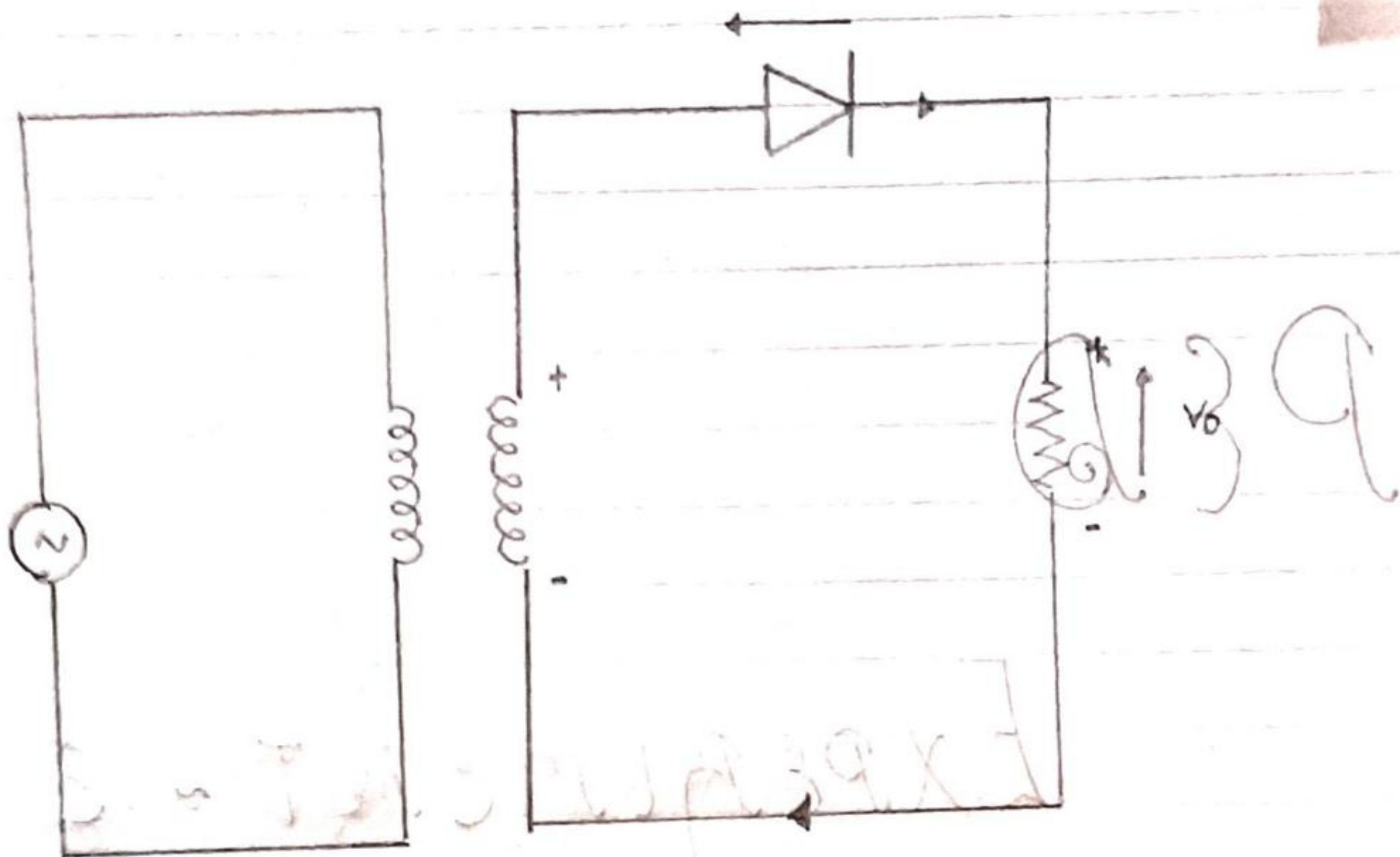

CKT DIAGRAM

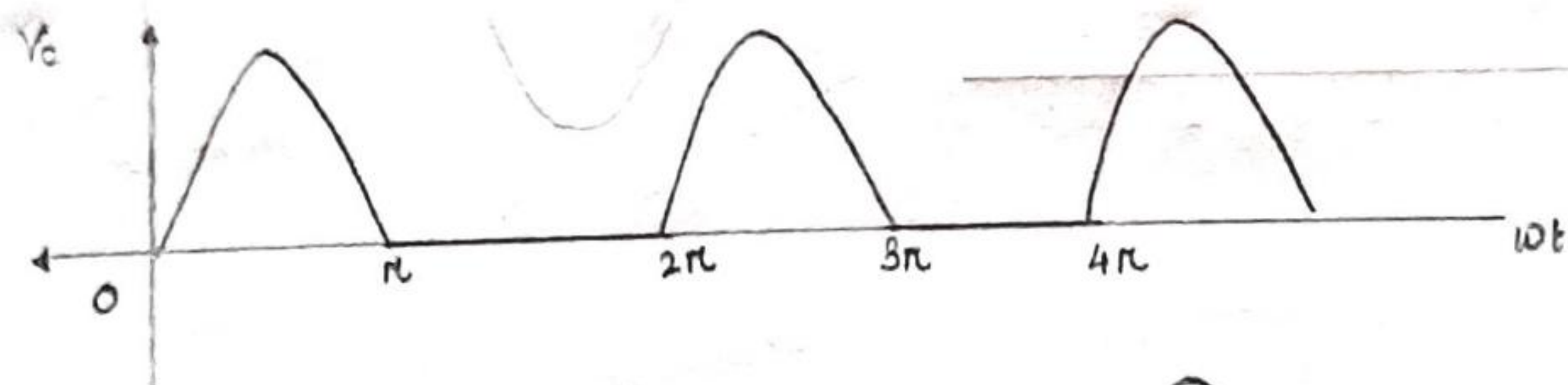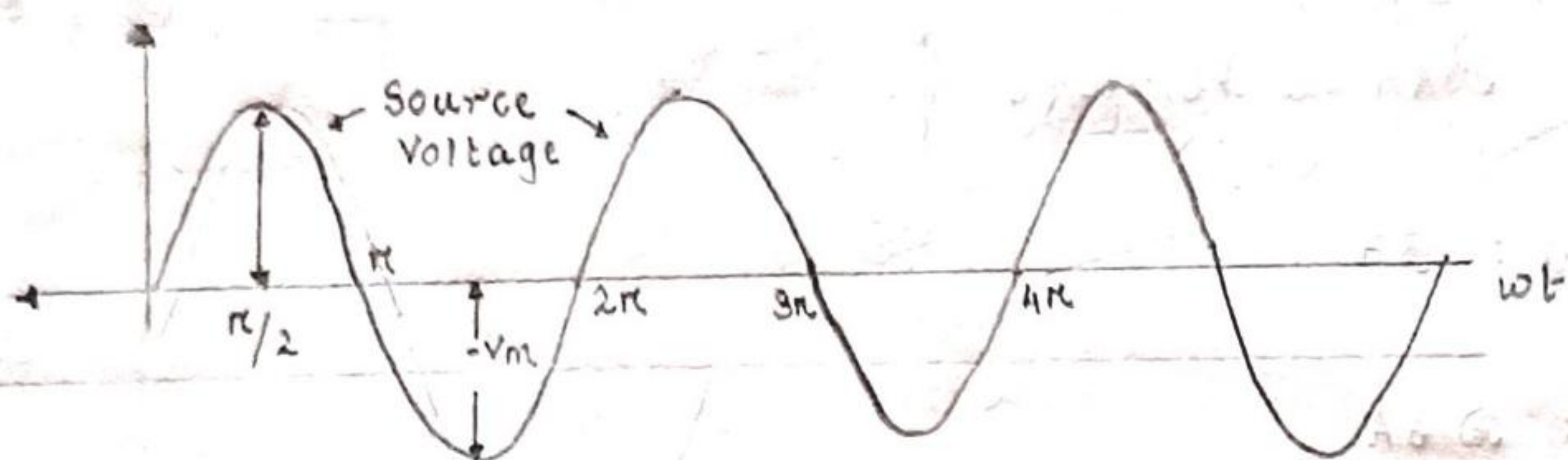

WAVEFORMS

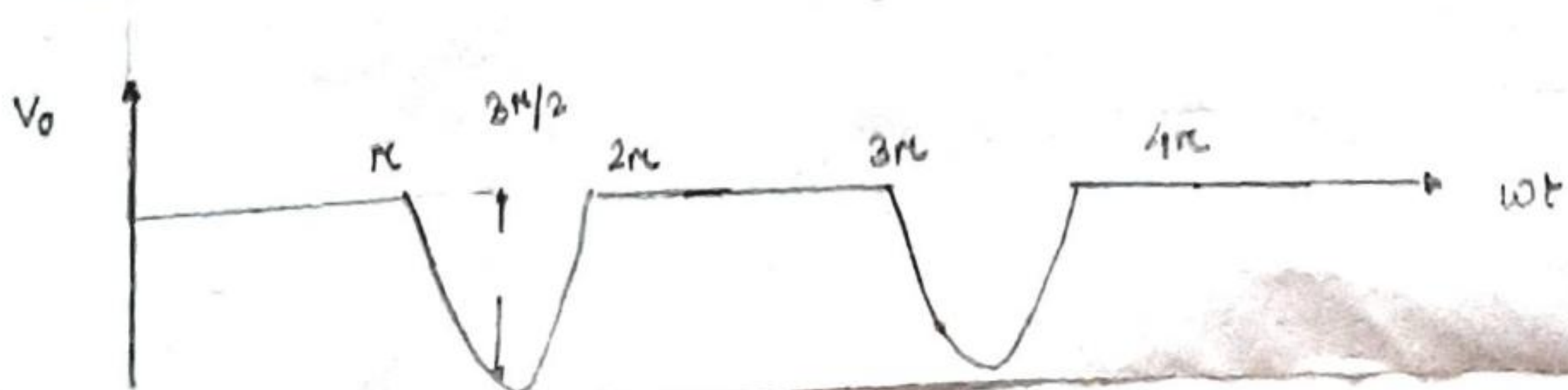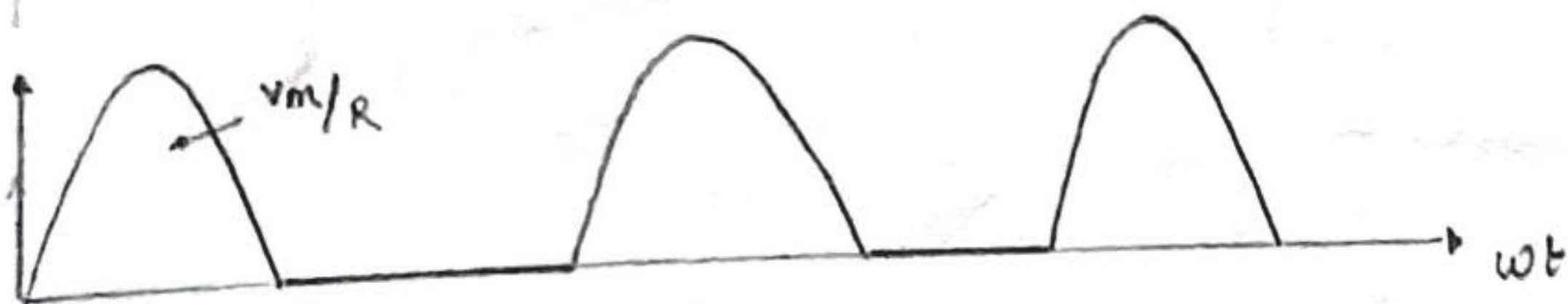



Aim: Simulate uncontrolled Half Wave & Full Wave Rectifier with  $R$  &  $R_L$  load.

Software Used: Multisim, Diode, Resistor & Inductor.

Theory:

i) Half - Wave Rectifier:

It is simplest type of uncontrolled rectifier. In single-phase half-wave rectifier for one cycle of supply voltage there is one half cycle of output or voltage. As such it is also called single-phase one-pulse rectifier. The load on the output side of rectifier may be  $R$ ,  $R_L$  or  $R_L$  with a flywheel diode.

a)  $R$  Load:

Ckt diagram of a single-phase half-wave rectifier is shown in

Fig a). During the +ve half cycle, diode is forward biased, it therefore conducts from  $\omega t = 0^\circ$  to  $\omega t = \pi$ . During the positive

half cycle o/p voltage  $V_o =$  source voltage  $V_s$  & load current

$I_o = V_o/R$ . At  $\omega t = \pi$ ,  $V_o = 0$  & for  $R$  load,  $I_o$  is also zero.

As soon as  $V_s$  tends to become negative after  $\omega t = \pi$ , diode

is reverse biased, it is therefore turned off & goes into





blocking state. Output Voltage as well as o/p current are

zero from  $\omega t = \pi$  to  $\omega t = 2\pi$ . After  $\omega t = 2\pi$ , diode is

again forward biased.


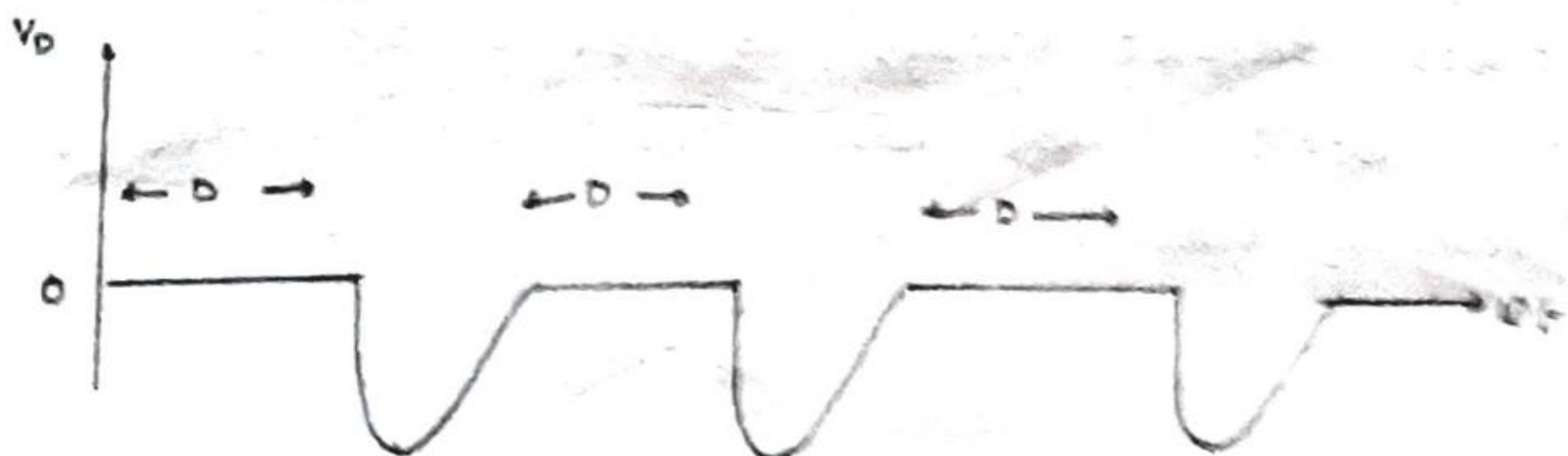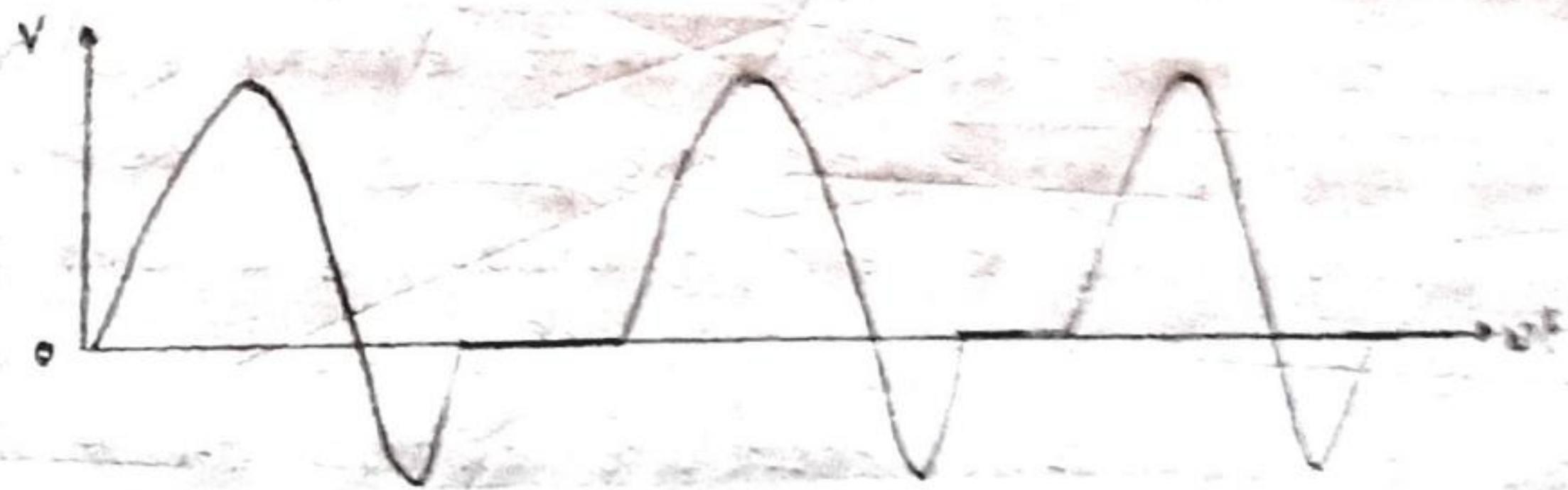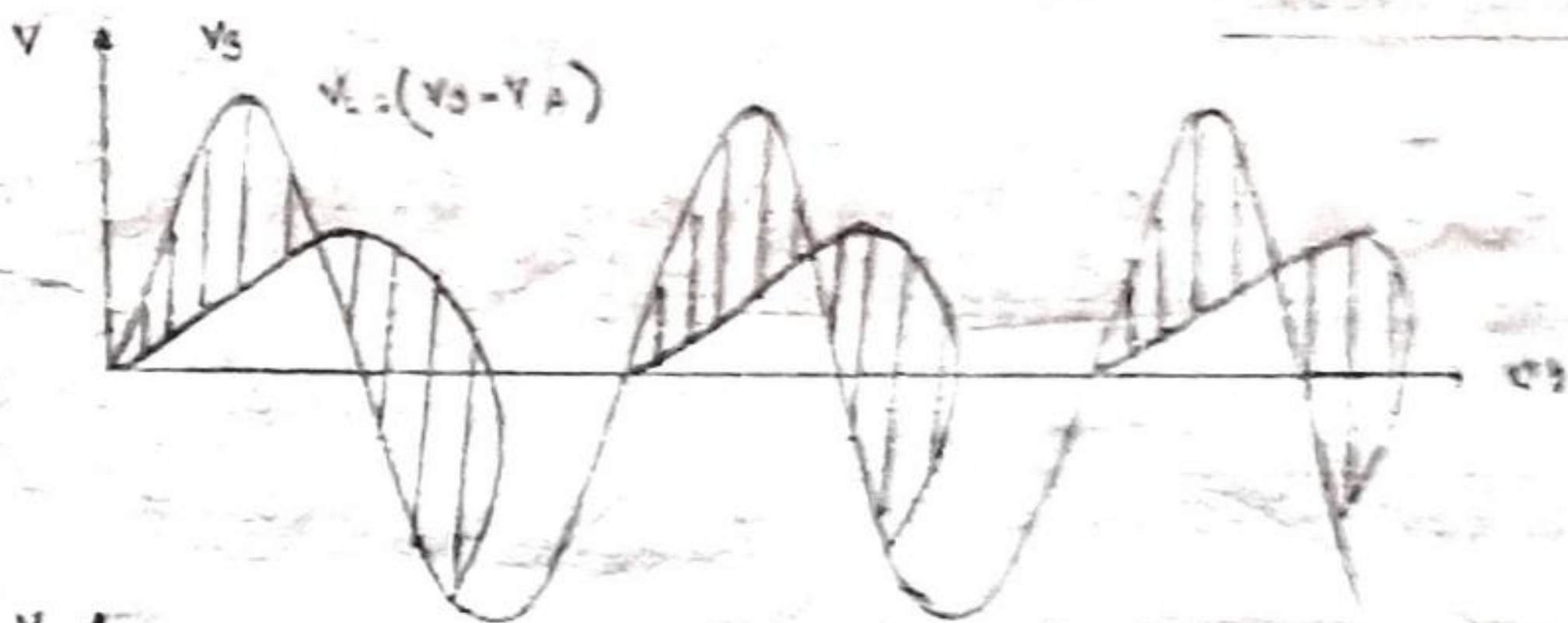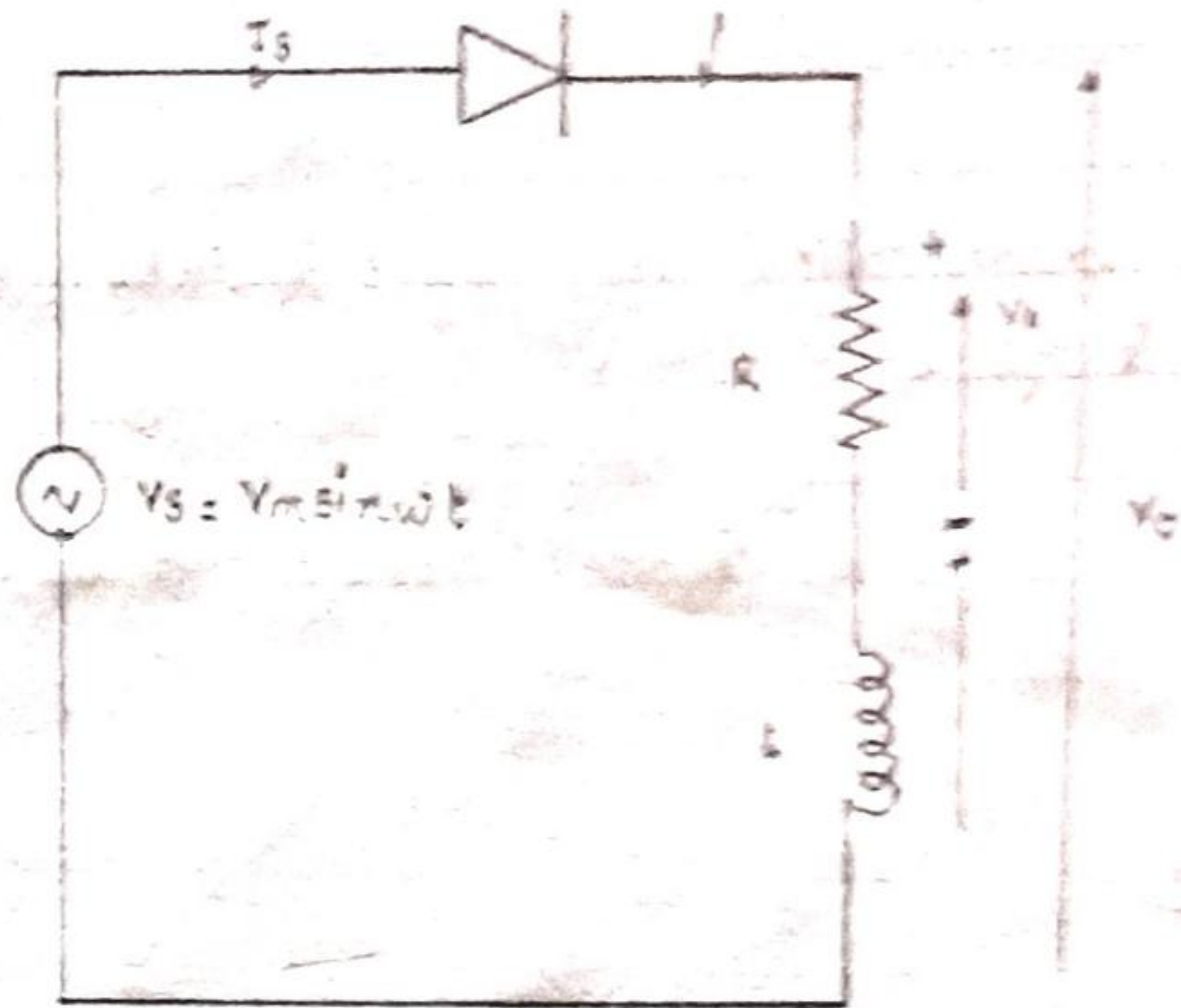
# SINGLE PHASE HALF WAVE DIODE RECTIFIER WITH RL LOAD





For a resistive load o/p current  $i_o$  has the same waveform as that of output voltage  $V_o$  diode voltage  $V_D$  is zero when diode conducts. Diode is reverse biased from  $\omega t = \pi$  to  $\omega t = 2\pi$ . The waveform of  $V_s$ ,  $V_o$ ,  $i_o$  &  $V_D$ . Here source voltage is sinusoidal  $V_s = V_m \sin \omega t$ . KVL for circuit gives  $V_s = V_o + V_D$ .

### FORMULAE :

i) Average value of output voltage

$$V_o = \frac{V_m}{\pi}$$

ii) RMS value of o/p voltage

$$V_{or} = \frac{V_m}{2}$$

iii) Average value of load current

$$I_o = \frac{V_o}{R} = \frac{V_m}{\pi R}$$

$$I_{or} = \frac{V_{or}}{R} = \frac{V_m}{2R}$$

Peak value of load, or diode current =  $\frac{V_m}{R}$

Peak Inverse voltage (PIV) is the maximum voltage that appears across the device during its blocking state.




$$PIV = V_m = \sqrt{2} V_s = \sqrt{2} (\text{rms value of transform second voltage})$$

Power Delivered to resistive load = (rms load voltage) (rms load current)



$$= V_{or} I_{or} = \frac{V_m}{2} \frac{V_m}{2R} = \frac{V_m^2}{4R} = \frac{V_s^2}{2R}$$


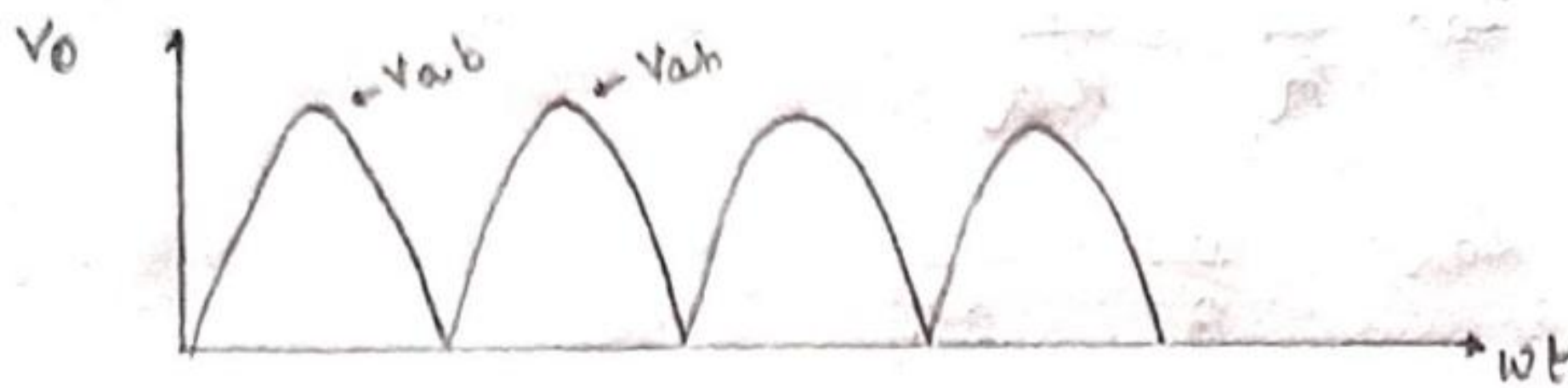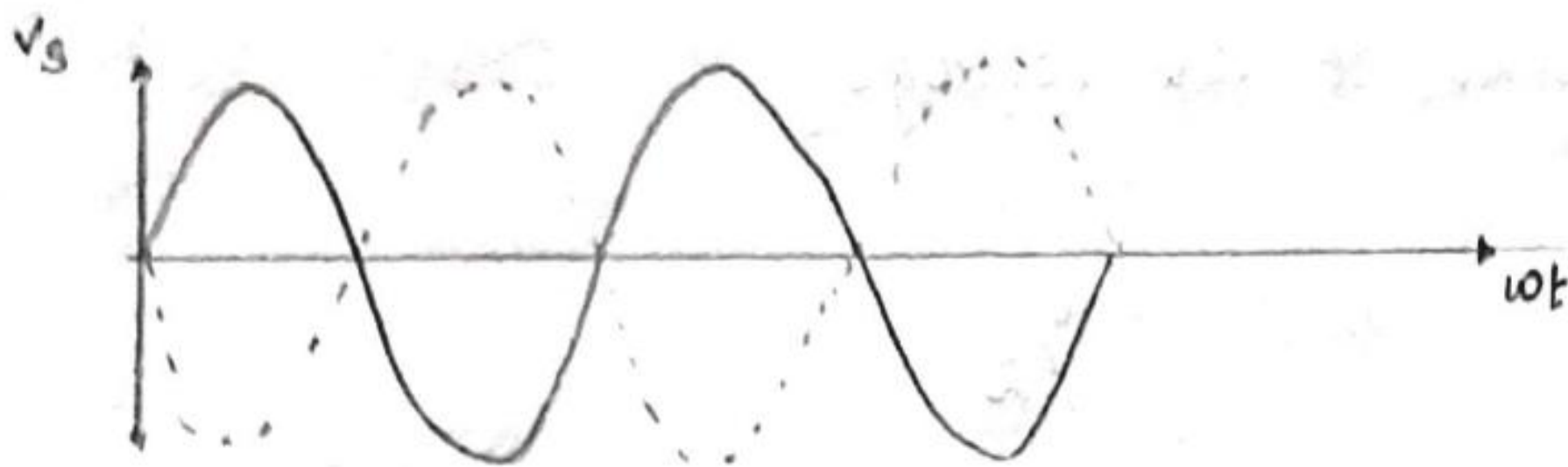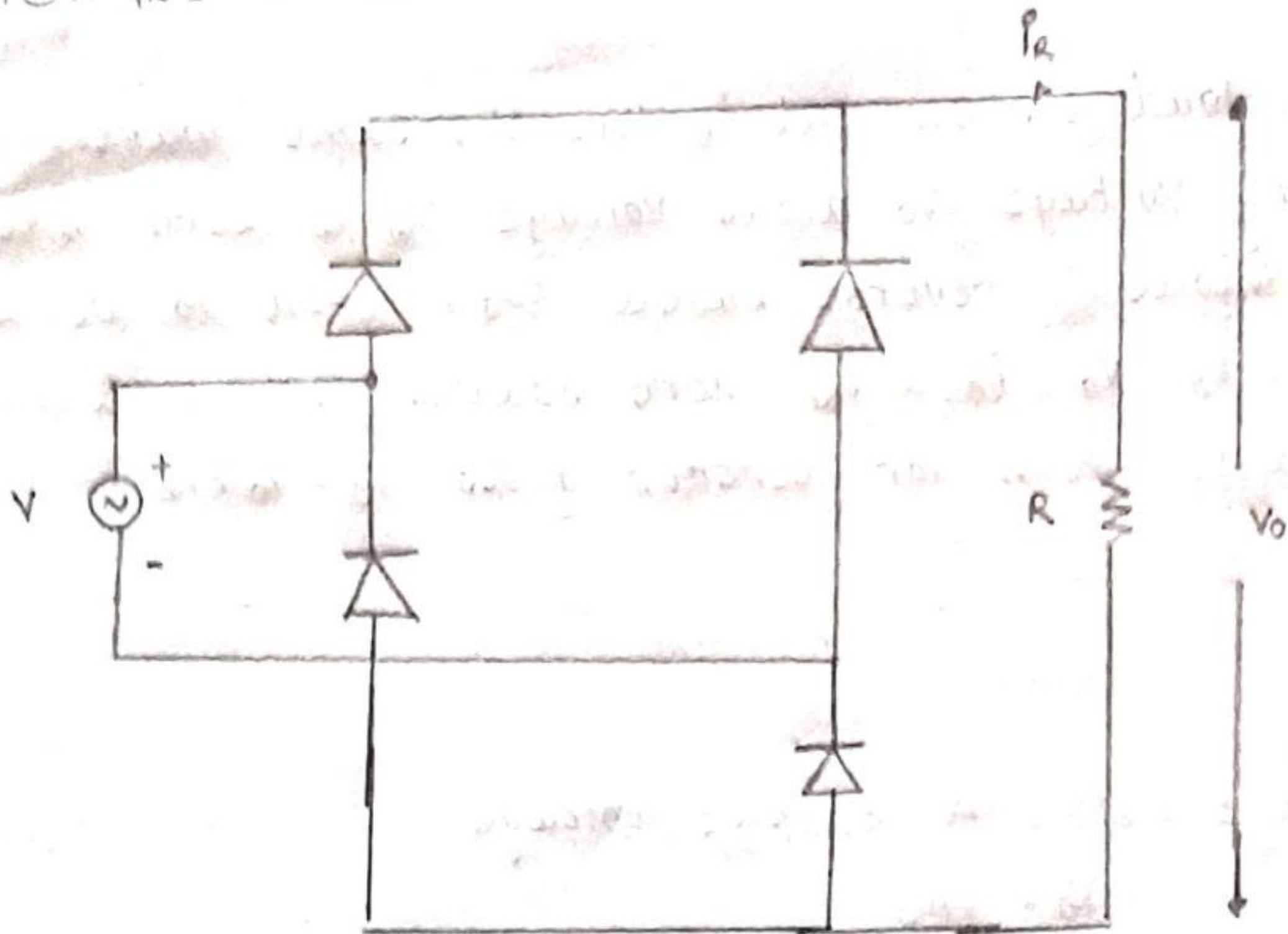
# SINGLE-PHASE FULL-WAVE DIODE BRIDGE RECTIFIER



WAVEFORMS

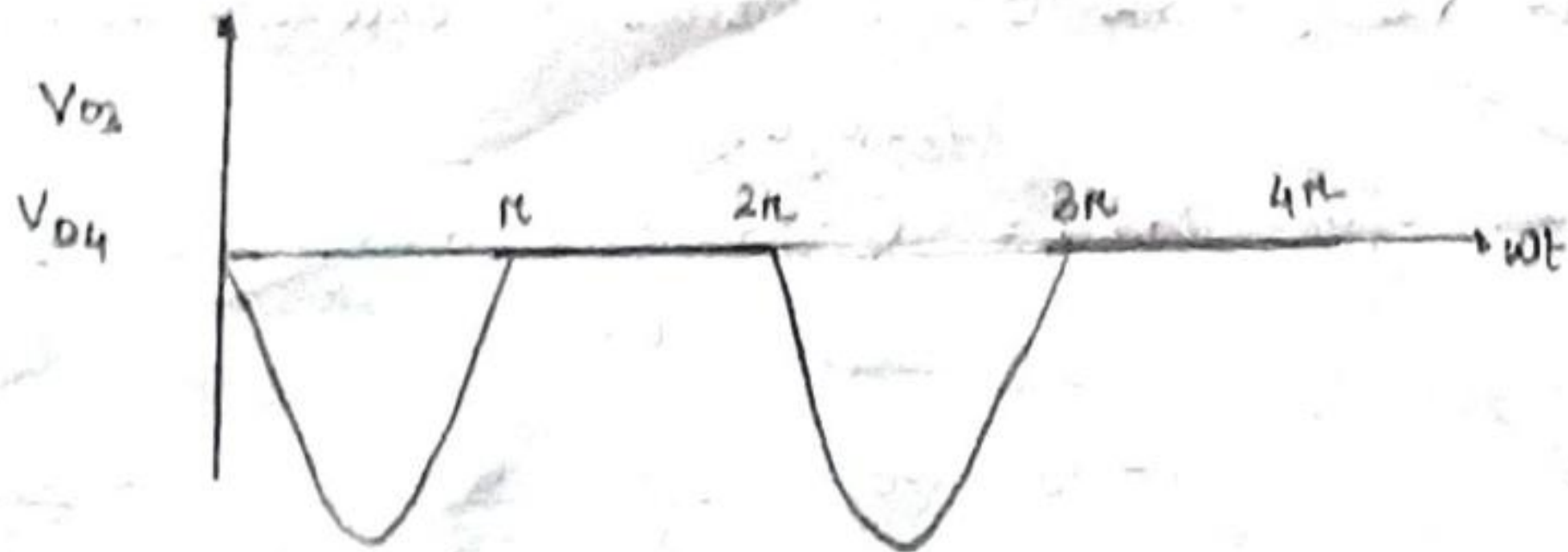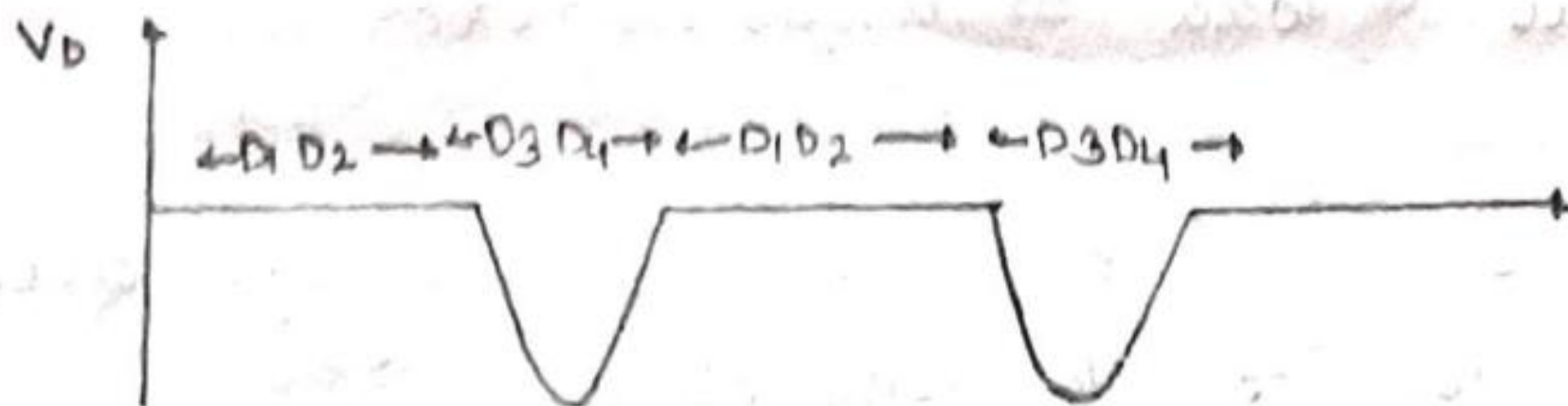



Input Power factor =  $\frac{\text{Power delivered to load}}{\text{Input } V_A} = \frac{V_{or} I_{or}}{V_s I_{or}} = \frac{V_{or}}{V_s} = 0.707109$

**RL load:** A single phase one-pulse diode rectifier feeding RL load. current continues to flow even after source voltage  $V_s$  has become negative, because of presence of inductance  $L$  in the load ckt. voltage  $V_A = I_o R$  has the same waveshape as that of  $I_o$ . Inductor voltage  $V_L = V_s - V_A$ . The current  $I_o$  flows till 2 areas A & B are equal. Area A represents the energy stored by  $L$  & area B the energy released by  $L$ . It must be noted that average value of voltage  $V_L$  across inductor  $L$  is zero. When  $I_o = 0$  at  $\omega t = \beta$ ;  $V_L = 0$ ,  $V_A = 0$  & voltage  $V_s$  appears as reverse bias across diode as shown. At  $\beta$ , voltage  $V_D$  across diode jumps from zero to  $V_m \sin \beta$  where  $\beta > \pi$ . Here  $\beta = \gamma$  is also the conduction angle of the diode.

Average value of o/p voltage =  $\frac{V_m (1 - \cos \beta)}{2\pi}$

Average value of load or o/p current  $I_o = \frac{V_o}{R} = \frac{V_m (1 - \cos \beta)}{2\pi R}$

ii) **Full-wave Rectifier:** A single-phase full wave bridge rectifier employing diodes is shown. When 'a' is +ve w.r.t 'b', diodes  $D_1, D_2$  conduct together so that o/p voltage is  $V_{ab}$ . Each of the diodes  $D_3$  &  $D_4$  is subjected to reverse voltage of  $V_s$ . When 'b' is +ve w.r.t to 'a', diodes  $D_3, D_4$  conduct together & output voltage  $V_{ba}$ . Each of the 2 diodes  $D_1$  &  $D_2$  experiences a reverse voltage of  $V_s$ .

**FORMULAE:** Average value of o/p is given by

$V_r = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d\omega t = \frac{V_m}{\pi} (1 - \cos \omega t_r)$

FOR EDUCATIONAL USE



Conclusion: Simulation of uncontrolled half & full wave rectifier have been executed successfully on Multisim and are well comprehended.