


Name: Rahul Vemuri

Roll No:33


Class:D16A

Experiment No. 2 A


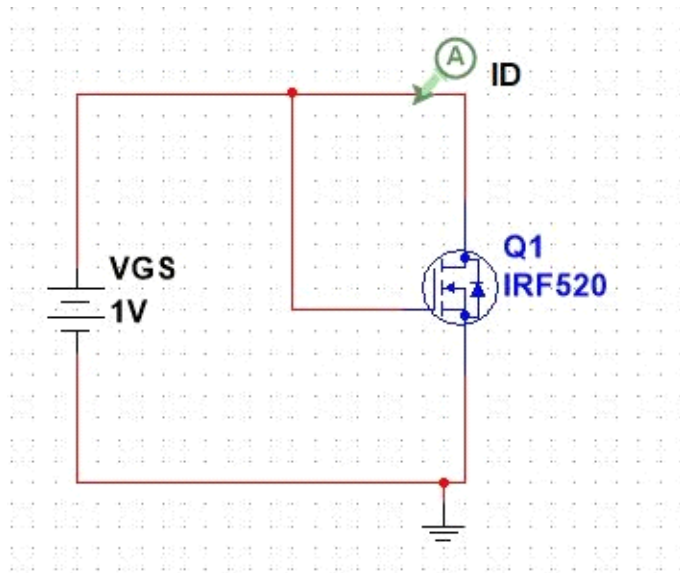
Aim: - To Simulate input and output of characteristics of Power MOSFET



Transfer characteristics

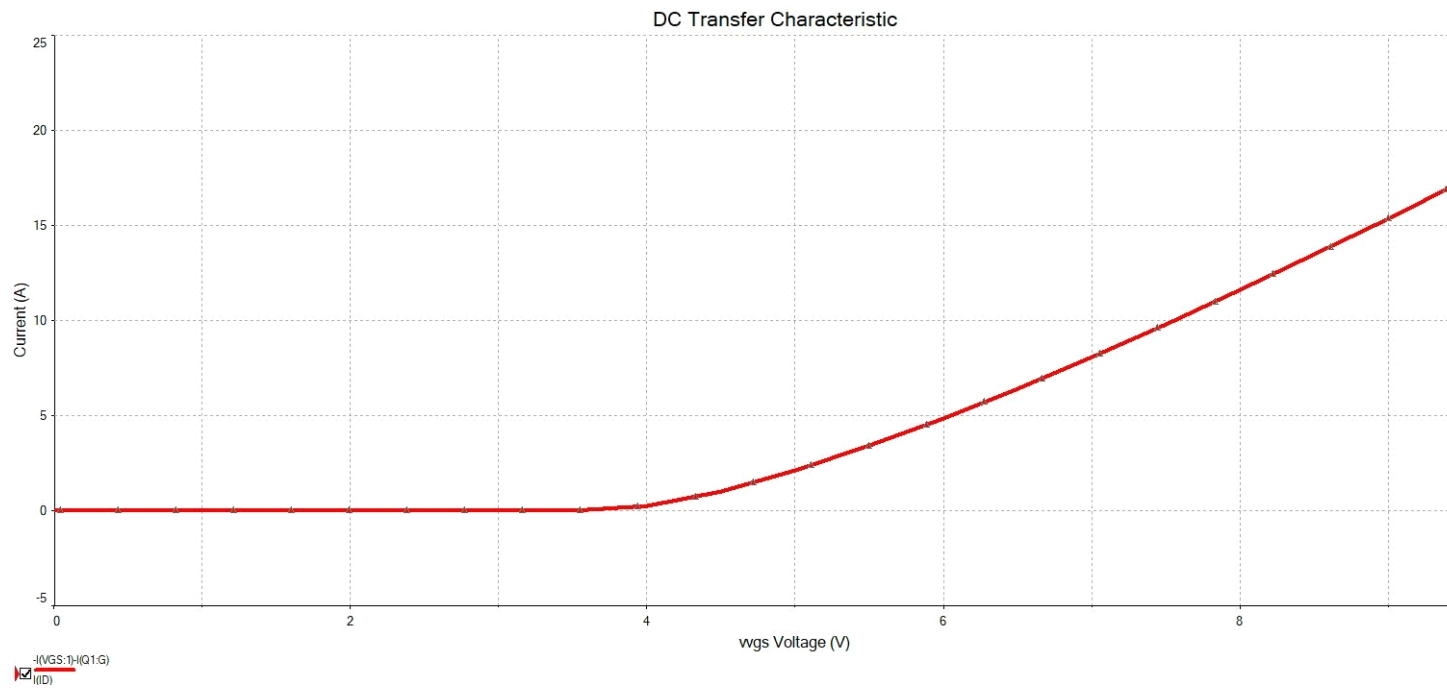

Output characteristics:

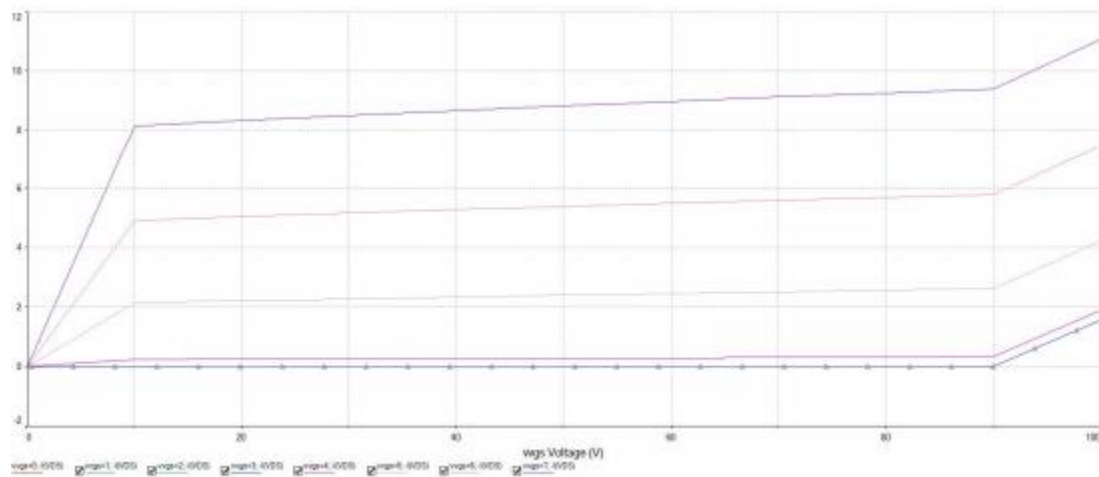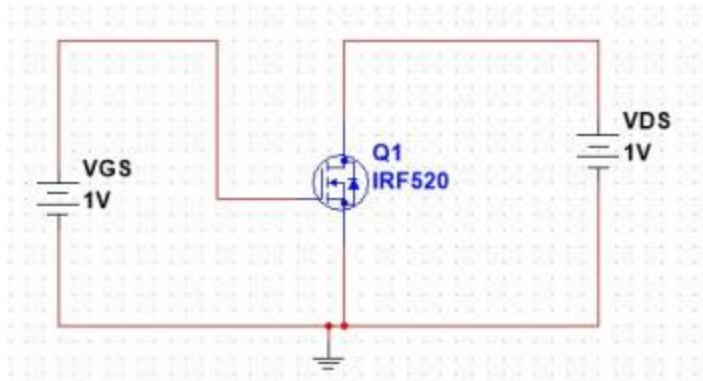

Experiment No. 2 B

Aim: - To Simulate input and output of characteristics of IGBT

Transfer characteristics

